

A note about course content, speed

- Class slides are meant to be an overview
 - We'll cover as much of the content as possible
 - Covering all topics in detail would take a semester-long class
 - Fastest route: memorization of questions/answers
- Recommendations:
 - Read the chapter(s) we're covering each week
 - Also review the relevant questions
 - In the ARRL book, look for notes like **[T7C06]** for relevant questions
 - In <https://hambook.org>, questions are included in the text
 - RECOMMENDATION: read the question, read ONLY the correct answer to associate the question with the answer

Table 2.1: International System of Units (SI) — Metric Units

PREFIX	SYMBOL	MULTIPLICATION FACTOR
Tera	T	$10^{12} = 1,000,000,000,000$
Giga	G	$10^9 = 1,000,000,000$
Mega	M	$10^6 = 1,000,000$
Kilo	k	$10^3 = 1000$
Hecto	h	$10^2 = 100$
Deca	da	$10^1 = 10$
Deci	d	$10^{-1} = 0.1$
Centi	c	$10^{-2} = 0.01$
Milli	m	$10^{-3} = 0.001$
Micro	μ	$10^{-6} = 0.000001$
Nano	n	$10^{-9} = 0.000000001$
Pico	p	$10^{-12} = 0.000000000001$

NOTE

$$10^{-1} = \frac{1}{10}$$

$$10^{-2} = \frac{1}{100}$$

$$10^{-3} = \frac{1}{1000}$$

Ohm's Law: $E=IR$

- **E**: voltage
 - Units – volts (V)
- **I**: current
 - Units – amperes (A)
- **R**: resistance
 - Units – ohms (Ω)

$$R = E / I$$

$$I = E / R$$

$$E = I \times R$$


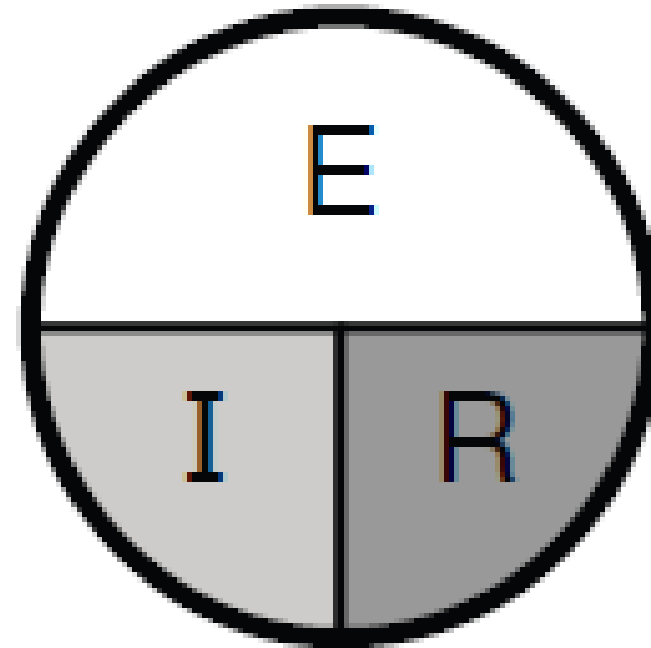


Figure 3.5A —If you know any two of the quantities, the equation to find the third — just cover up the unknown quantity. The positions of the remaining two symbols show if you have to multiply (side-by-side) or divide (one above the other).


Examples of how to use Ohm's Law

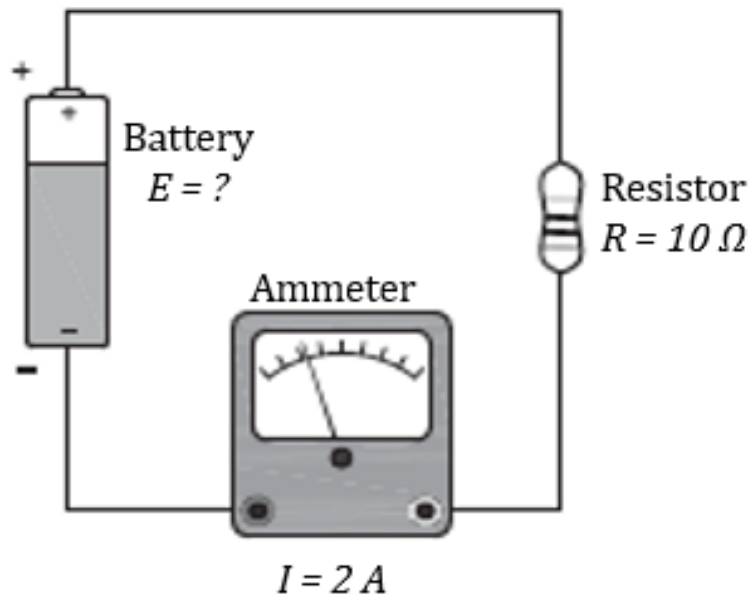

Given $I = 2$ Amperes
 $R = 10$ Ohms

Find: E (voltage)

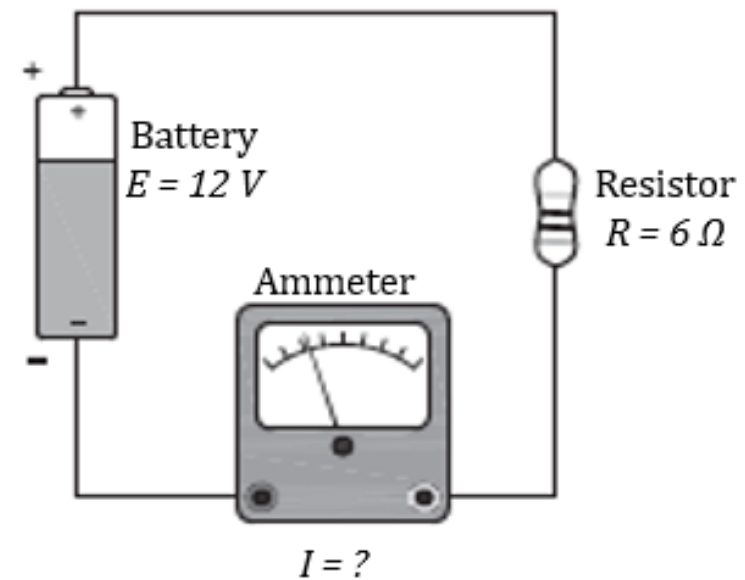$E = I \times R = 2 \times 10 = 20$ Volts
Voltage Equals 20 Volts



Given $E = 12$ Volts
 $R = 6$ Ohms

Find: I (current)

$I = E / R = 12 / 6 = 2$ Amps

Current Equals 2 Amperes

More Ohm's Law Examples

What is the resistance of a circuit in which a current of 3 amperes flows when connected to 90 volts?

$$R = E / I = 90 \text{ V} / 3 \text{ A} = 30 \Omega$$

What is the current in a circuit with an applied voltage of 120 volts and a resistance of 80 ohms?

$$I = E / R = 120 \text{ V} / 80 \Omega = 1.5 \text{ A}$$

What is the voltage across a 2-ohm resistor if a current of 0.5 amperes flows through it?

$$E = I \times R = 0.5 \text{ A} \times 2 \Omega = 1 \text{ V}$$

Power

- *Power*, represented by the symbol P, is the rate at which electrical energy is used
 - Measured in *watts* (W)
- A device that consumes or dissipates power is referred to as a *load*

$$P = I \times E$$

$$E = P / I$$

$$I = P / E$$

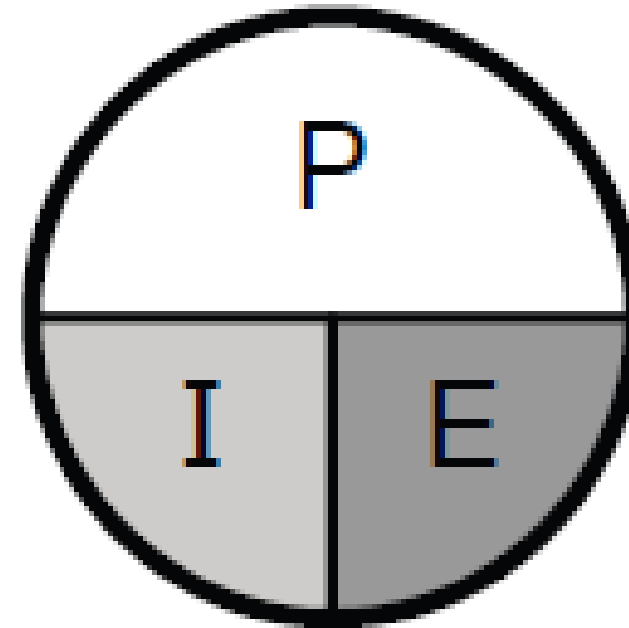


Figure 3.5B — Simple diagram to help remember the Ohm's Law. If you know any two of the quantities, the equation to find the third — just cover up the unknown quantity. The positions of the remaining two symbols show if you have to multiply (side-by-side) or divide (one above the other).

Example Power Calculations

How much power is delivered by a voltage of 13.8 volts DC and a current of 10 amperes?


$$P = E \times I = 13.8 \text{ V} \times 10 \text{ A} = 138 \text{ W}$$

How much current is required to deliver 120 watts at a voltage of 12 volts DC?

$$I = P / E = 120 \text{ W} / 12 \text{ V} = 10 \text{ A}$$

Components and Units

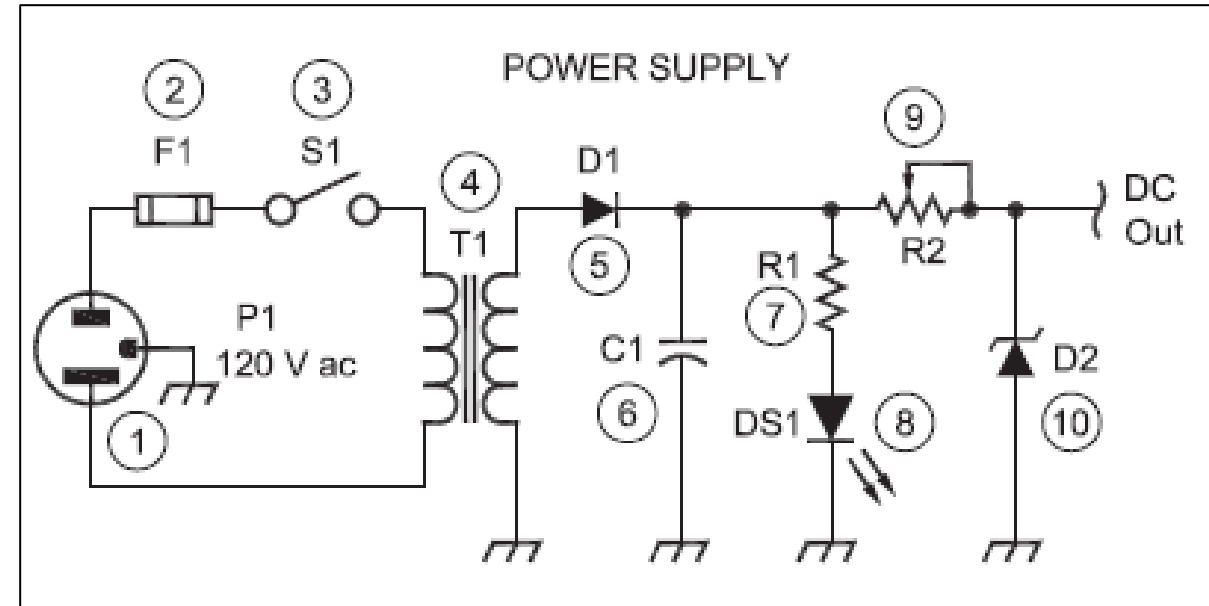- Components in electrical circuits performs functions such as storing or using energy, routing current, or amplifying signals
- The three most basic types of electronic components are **resistors**, **capacitors** and **inductors**
- **Schematic diagrams** are a convenient shorthand for complex circuits



More on schematics later ...



Resistors

- Function: To restrict the flow of current, like a valve in a water pipe
- Resistance measured in ohms (Ω)
- Remember Ohm's Law ($R = \text{resistance}$)

$$I = E / R$$

$$E = I \times R$$

$$R = E / I$$

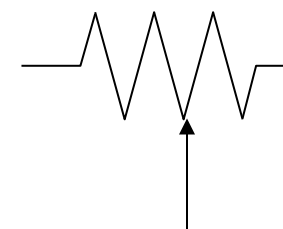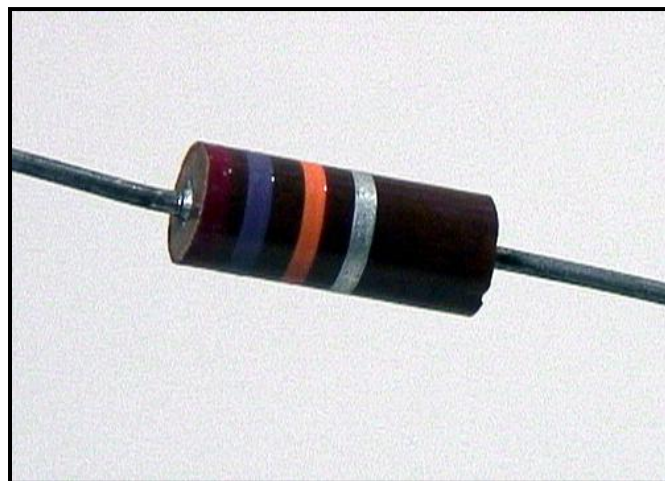

Potentiometer
or "Pot"

Arrow indicates adjustable
value, such as for a volume
control.

Resistor Schematic




Large Variety of Resistors!



Capacitors

- The function of a capacitor is to store electrical energy – called *capacitance*
 - Capacitance measured in *farads (F)*
- Acts like a short-term battery

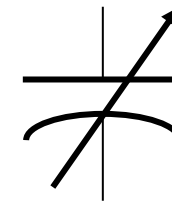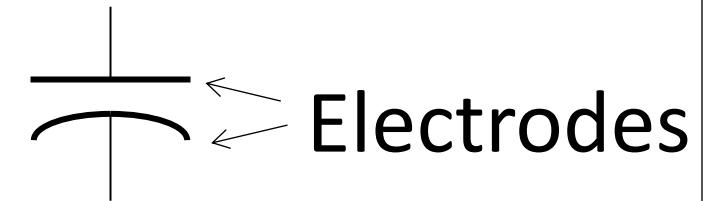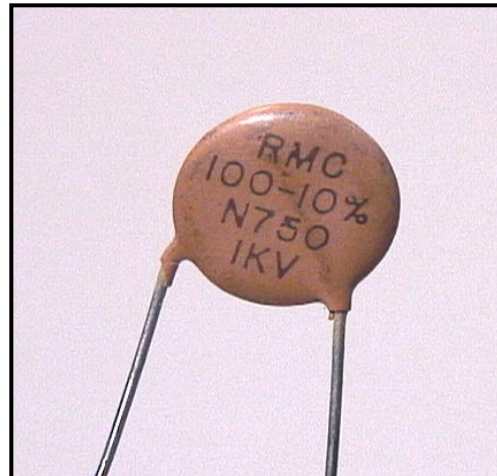
*Stores energy in an **electric field** created by voltage between the electrodes with insulating **dielectric** material between them*



Schematic


Inductors

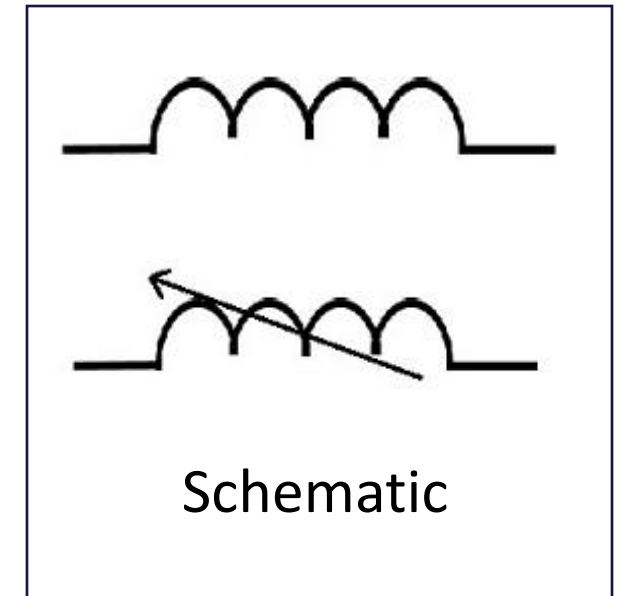- Function: To store energy in the magnetic field created by current flowing in a wire
 - Called *inductance*, measured in *henrys* (H)
- Made from wire wound in a coil, sometimes around a core of magnetic material that concentrates the magnetic energy





Variable Components

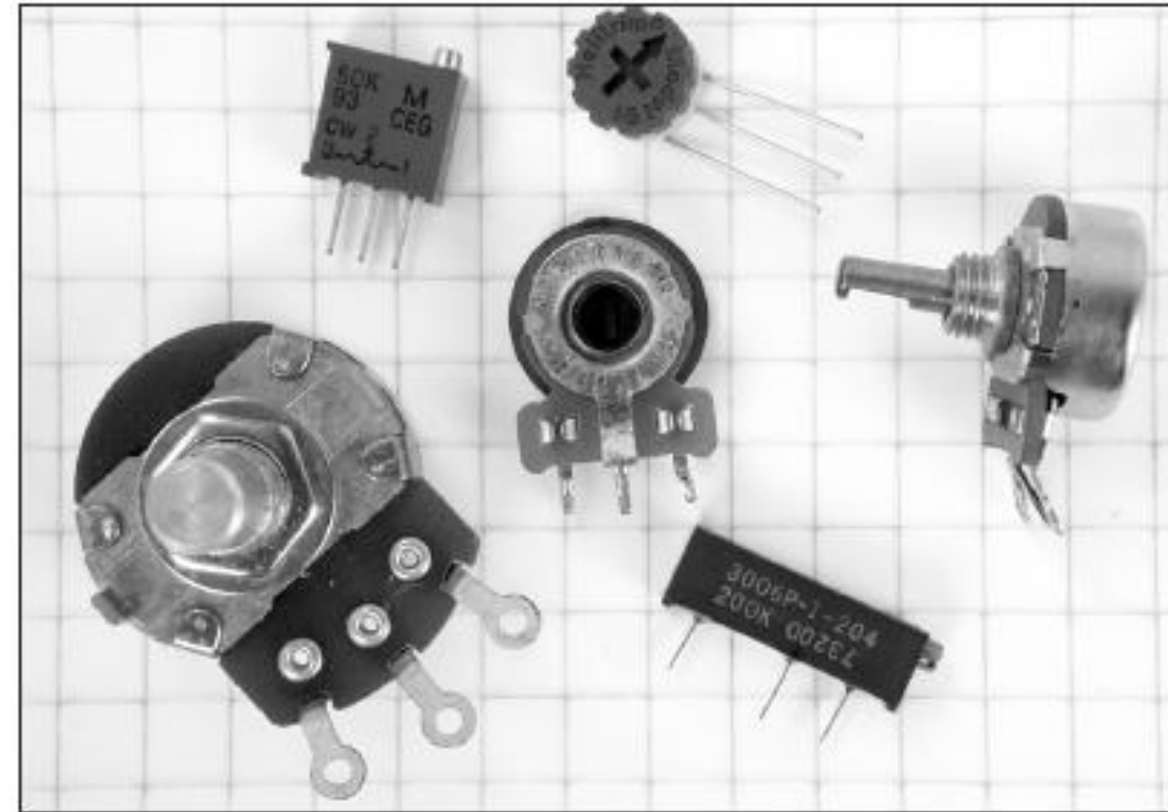- All three types of basic components are also available as adjustable or variable models
- A variable resistor is also called a *potentiometer*, frequently used to adjust voltage or potential, such as for a volume control



Transformers

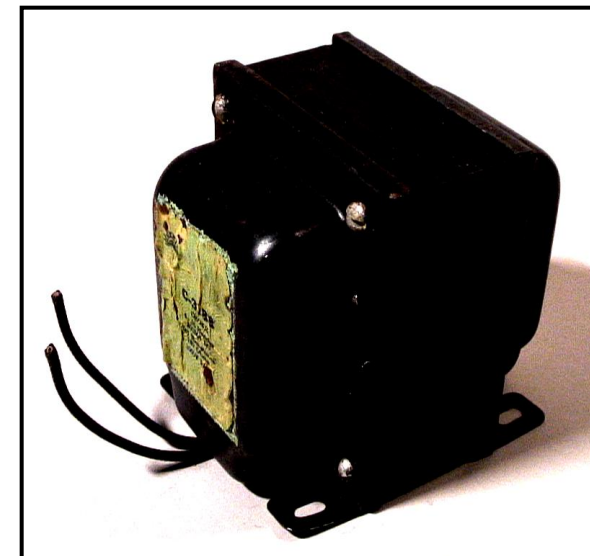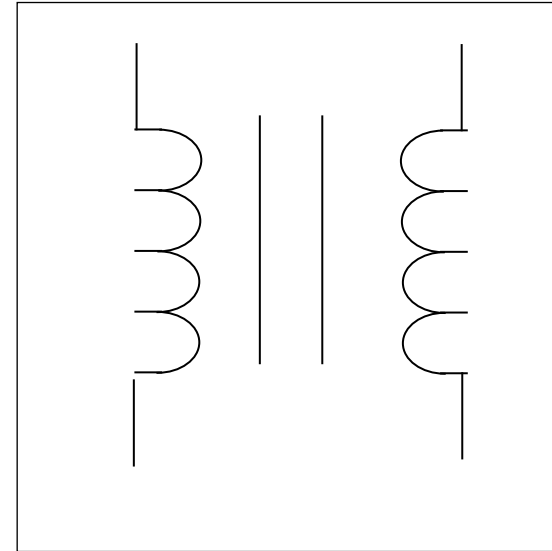- Made from two or more inductors that share their stored energy
 - Transfer energy from one inductor to another, but change voltage and current
- Example: laptop charging brick
 - Transfer energy from 120V AC to a lower voltage and current



Reactance and Impedance

- In a resistor, AC voltages and currents are exactly in step, or *in phase*
- In capacitors and inductors, voltage and current have a *phase difference*
 - Capacitors and inductors store energy, resistors dissipate energy
- Energy storage creates an effect called *reactance* (symbol X) that acts like a resistance in opposing the flow of AC current
 - Capacitors create *capacitive reactance* (X_C)
 - Inductors create *inductive reactance* (X_L)
 - The effects of each are complementary

Reactance and Impedance (cont.)



- The combination of *resistance* (R) and *reactance* (X) is called *impedance*, represented by the symbol Z (units: ohms)
 - Impedance represents a circuit's *opposition* to **both** AC and DC currents
- Radio circuits almost always have both resistance and reactance, so impedance is often used as a general term to mean the circuit's opposition to AC current flow

Resonance

- Circuits that contain both a capacitor and an inductor are called *resonant* circuits or *tuned* circuits
- A component's reactance depends on frequency
 - Inductive reactance (X_L) increases with frequency, capacitive reactance (X_C) decreases
- At the frequency for which a circuit's X_L and X_C are *equal*, their effects cancel
 - This is the circuit's *resonant frequency*
- At *resonance*, a circuit has *only resistance*, which affects AC and DC current equally
- A tuned circuit acts as a *filter*
 - A filter passes or rejects signals at its resonant frequency
 - Useful for radios to filter out unwanted signals!

Resonant or Tuned Circuit

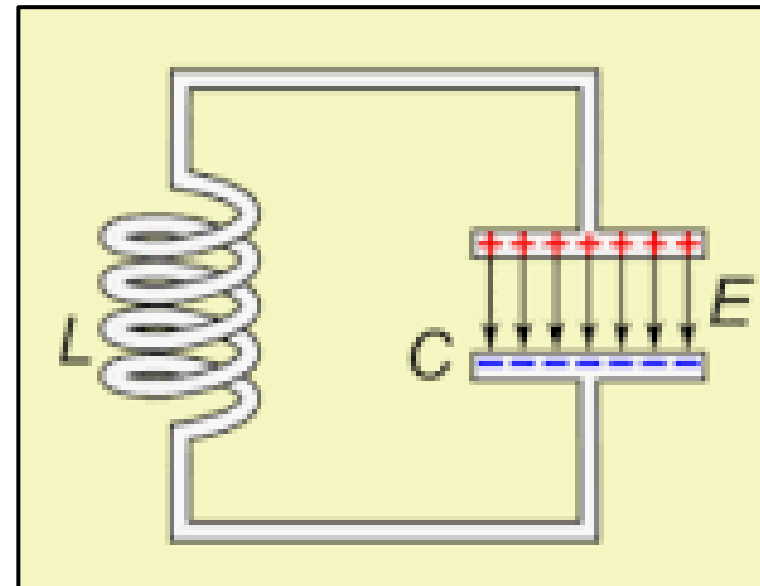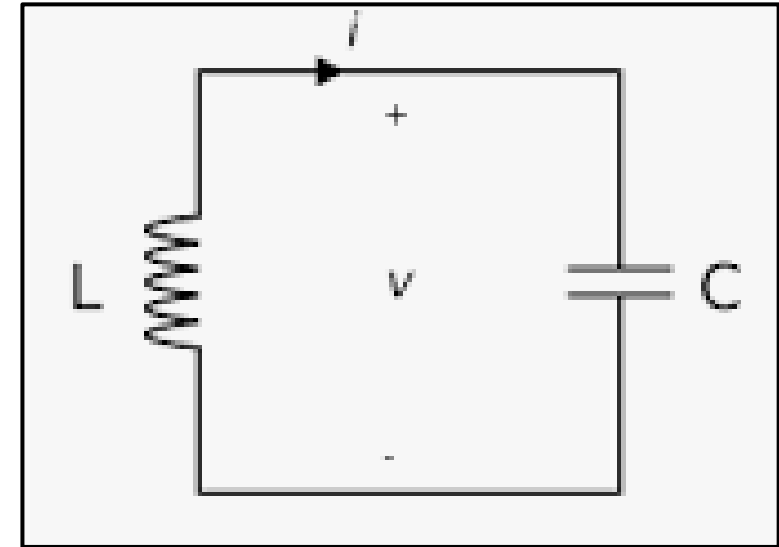- *Capacitors* and *inductors* connected together create a tuned circuit
- When X_L and X_C are equal, the circuit is resonant
- If C or L are adjustable, the resonant frequency can be varied or *tuned*



Diodes, Transistors and Integrated Circuits


(Semiconductors)

- Components made of “OK” conductors (not metals)
 - ***N-Type semiconductors***: made from materials with more electrons
 - ***P-Type semiconductors***: made from materials with fewer electrons
- Structures of N and P material can control current flow
- When N- and P-type material are placed in contact with each other, the result is a ***PN junction*** that conducts better in one direction than the other

Diodes



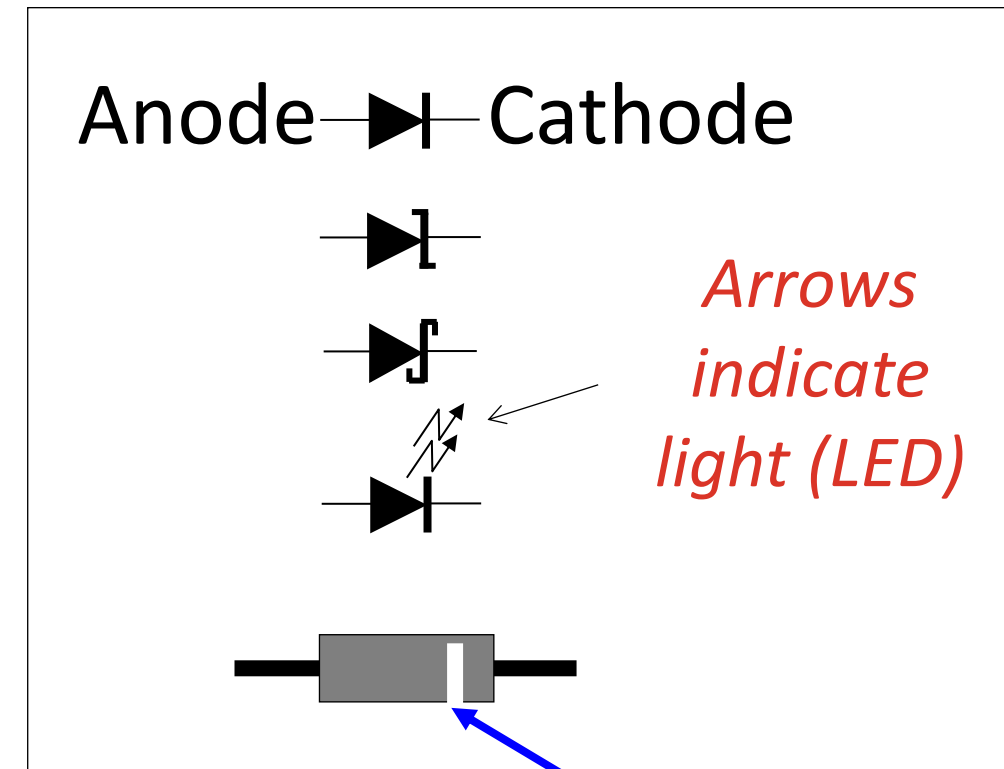
- One-way Current
 - Two electrodes (Anode, Cathode)
 - AC current is changed to varying pulses of DC (called *rectification*)
 - Diodes used to change AC power to DC power are called *rectifiers* (heavy-duty diodes)
- Designator (D or CR)
- If AC voltage is applied to a diode, the result is a pulsing DC current
 - Current is blocked when the voltage tries to push electrons in the wrong direction




Diodes (cont.)

- When current flows through a diode, a small positive voltage develops from the anode to the cathode
 - Called *forward voltage drop*, usually less than 1 V
 - Voltage depends on the type of diode and the materials it's made from
- Light-emitting diode or *LED* gives off light when current flows through it in the forward direction from anode to cathode
 - Used as visual indicators (use less power than incandescent bulbs/lamps)
 - Material from which the LED is made determines the color of light


Anode  Cathode

Transistors

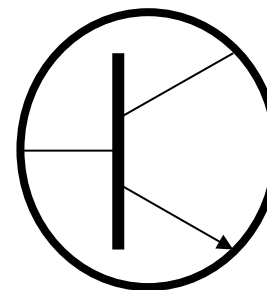- The function of a transistor is to *control* large signals with small ones
 - An “electronically controlled current valve”
 - When used as an amplifier, a transistor produces *gain*
 - Transistors can also be used as a *switch*
- Designator (Q)




Bipolar Junction
Transistor (BJT)

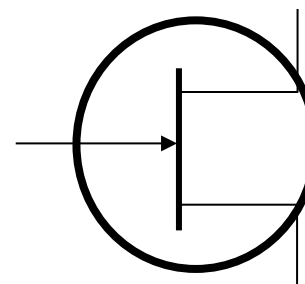

Field-Effect
Transistor (FET)

Transistors (cont.)


- Two common types of transistors: *bipolar junction transistors* (BJT) and *field effect transistors* (FET)
- The Bipolar Junction Transistor (BJT) has three layers of N or P material connected to electrodes
- Depending on the arrangement of layers, a BJT is either an NPN or PNP transistor
- The three electrodes of an FET are the *gate*, *drain*, and *source*
- RF power transistors are used as the primary gain-producing component in RF power amplifiers

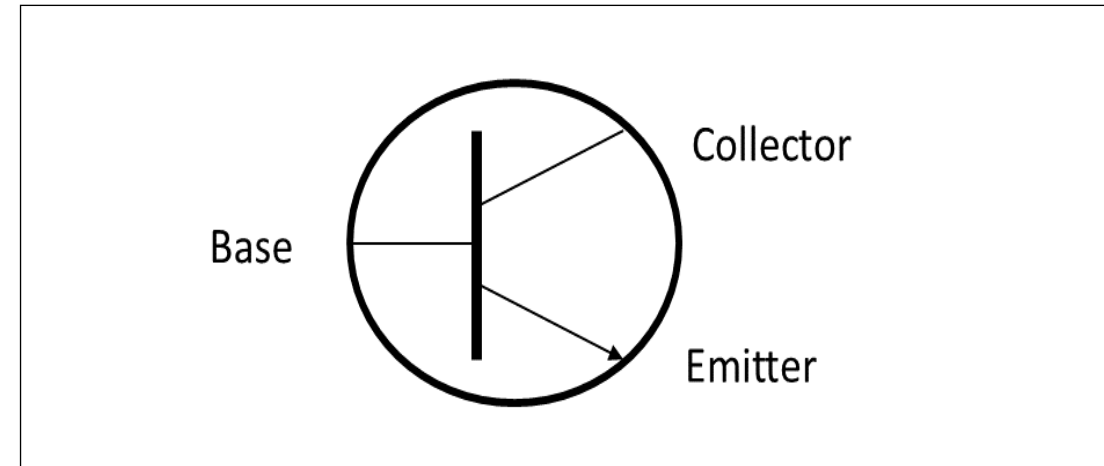

*Bipolar Junction Transistor Schematic
(showing the 3 electrodes)*



Transistors (cont.)

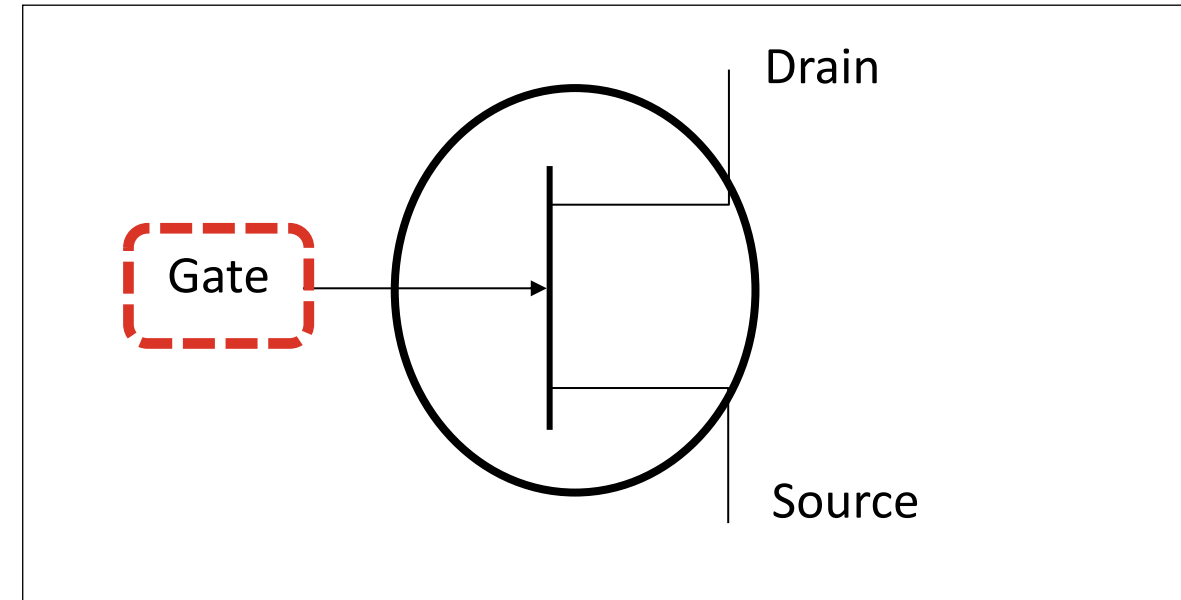- The Field-Effect Transistor (FET) has a conducting path or channel of N and P material connected to the drain and source electrodes
- Voltage applied to the **gate** electrode controls current through the channel



Integrated Circuits

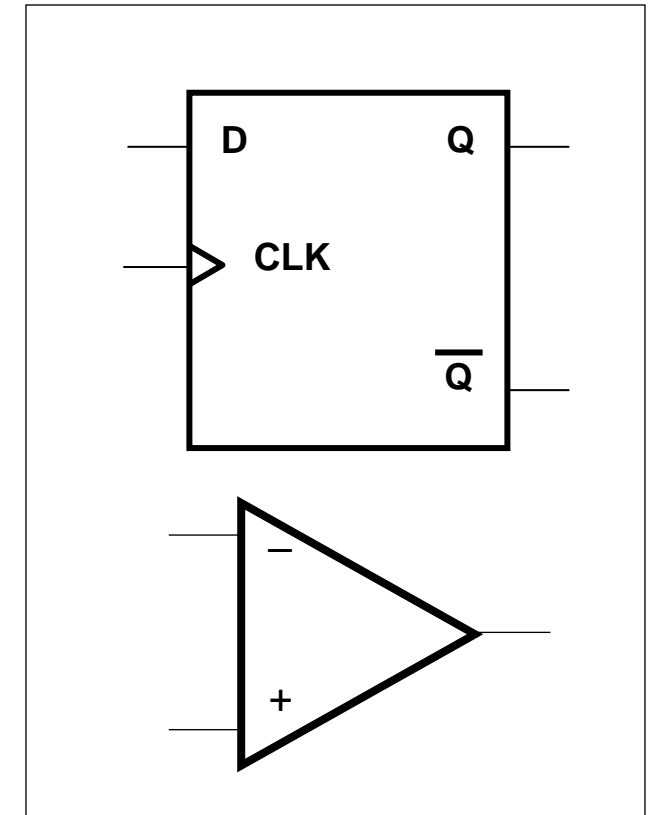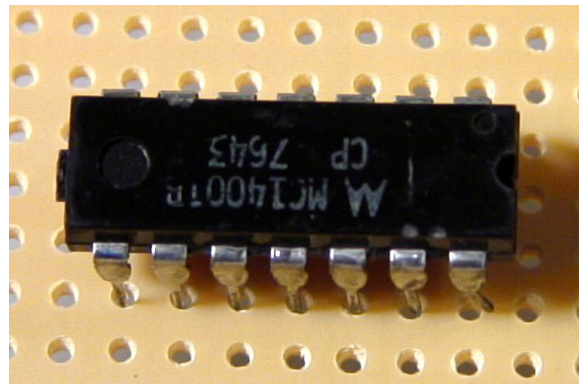- An integrated circuit (IC or chip) is made of many components connected together as a useful circuit and packaged as a single component
- Designator (IC or U)



Protective Components

- Protective components (such as *fuses* and *circuit breakers*) are used to prevent equipment damage or safety hazards such as fire or electrical shock
- Designed to remove power in case of a circuit *overload*
 - Fuses blow – one time protection
 - Short length of metal is melted when circuit overloaded, which breaks the circuit
 - Circuit breakers trip – can be reset and reused
- Important: ***use the correct current rating!***
 - Replacing with a higher current rating could damage equipment or start a fire



Fuses




Circuit
Breaker



Schematics



Circuit Breaker

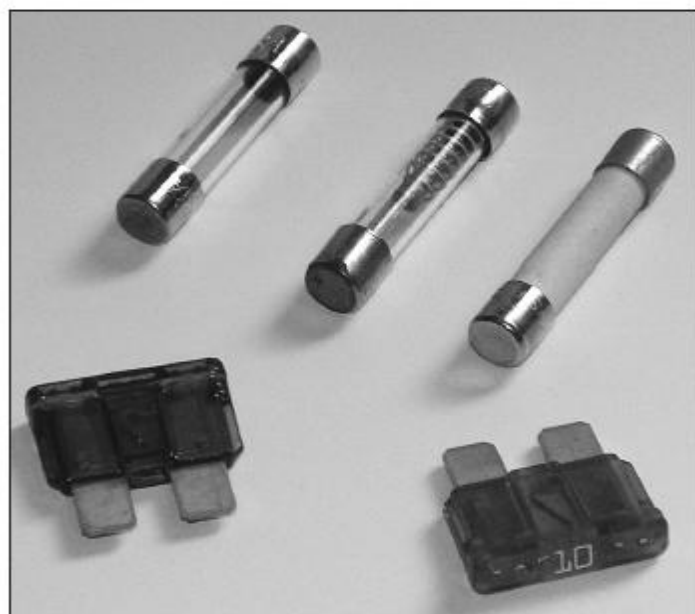

Fuses




Ground Fault
Circuit Interrupter
(GFCI) circuit
breaker



Circuit Gatekeepers ... Switches & Relays

- *Switches* and *relays* control current through a circuit by connecting and disconnecting paths for current to follow
- Switches and relays are described by # poles, # throws
 - The combination of poles and throws describes the switch
 - Each circuit controlled by the switch is a *pole*
 - Each position is called a *throw*
- Switches are operated manually
- Relays are controlled electronically by electromagnet

Switch Configurations

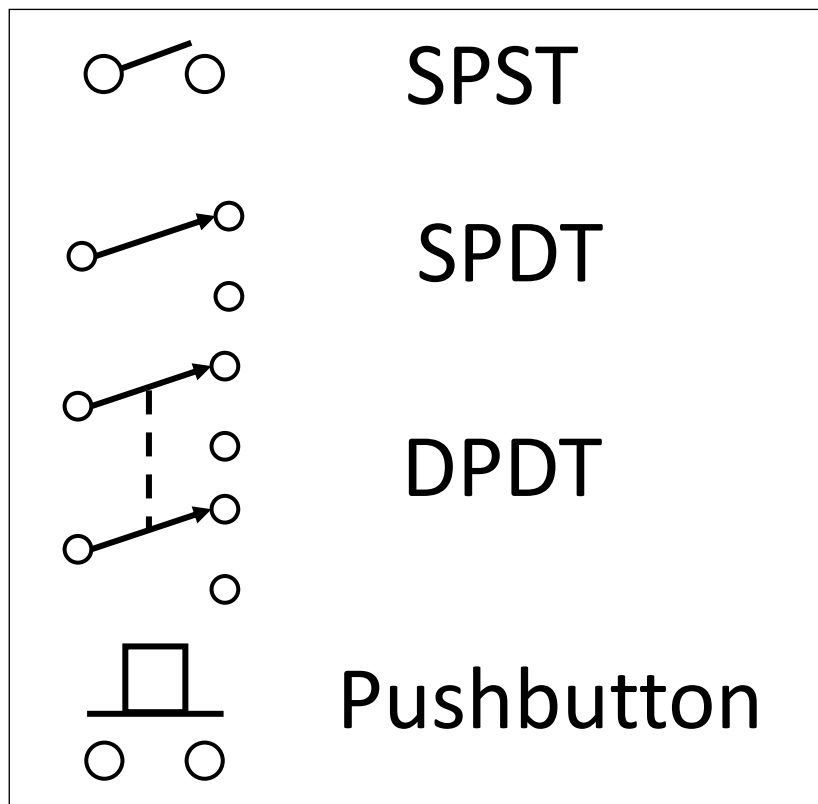

Switches

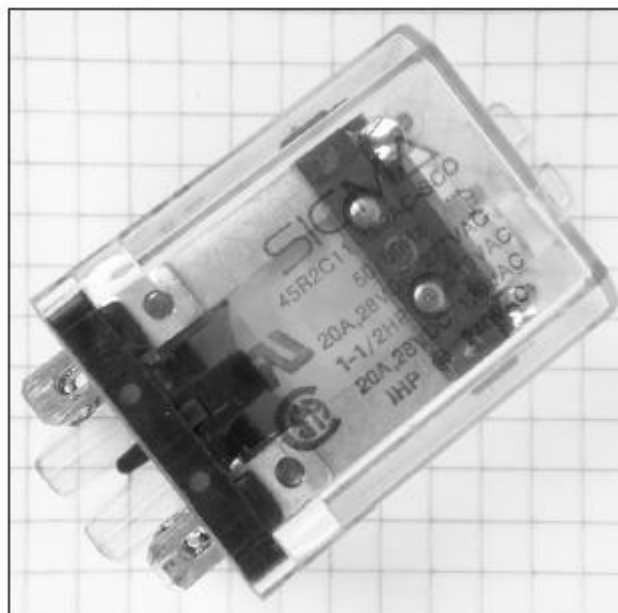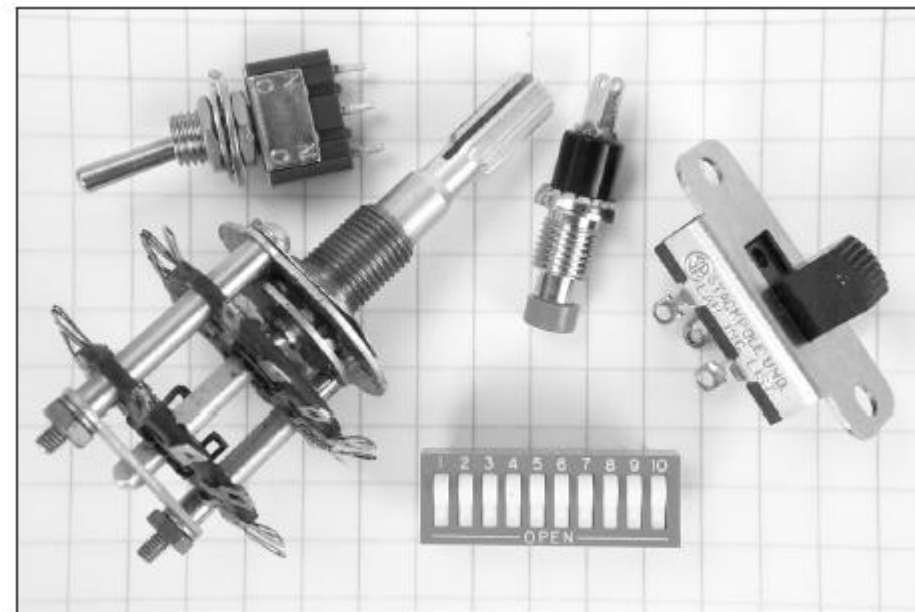

Relay

Indicator, Meters and Displays

- **Indicators** and **displays** are important components for radio equipment
 - An *indicator* is either **ON** or **OFF**
- A *meter* provides information as a numeric value
- A *display* combines indicators, numbers, and labels
 - A *liquid crystal display* or **LCD** is used on the front panel of many radios and test instruments

Fig 3.15 – Schematic Symbols (see text)



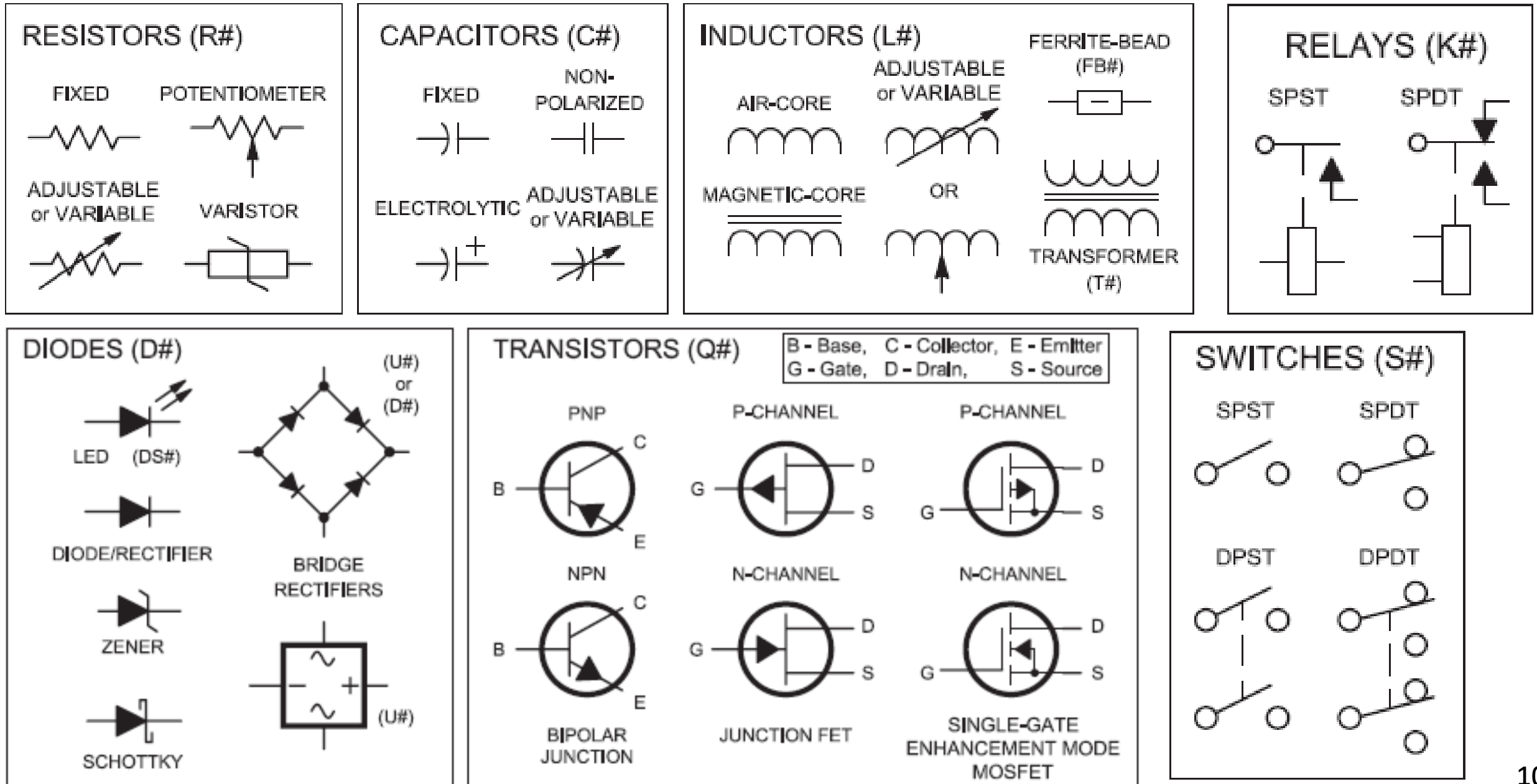
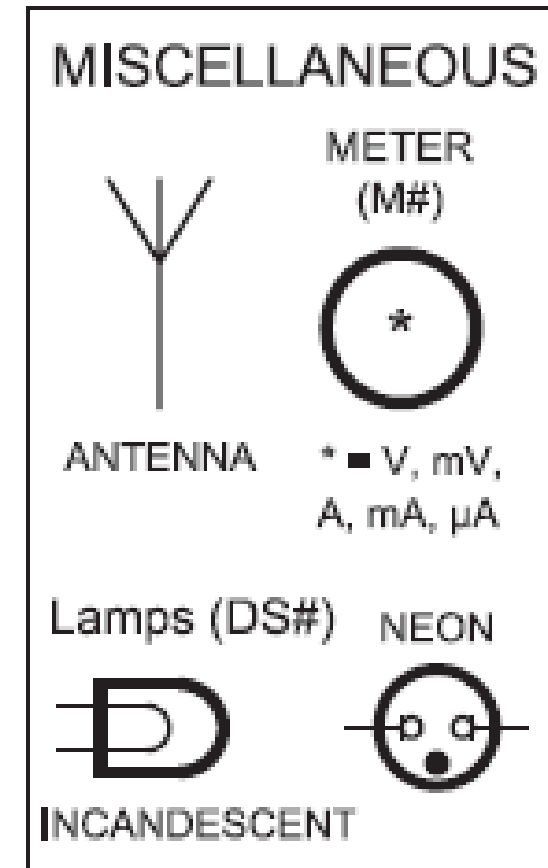
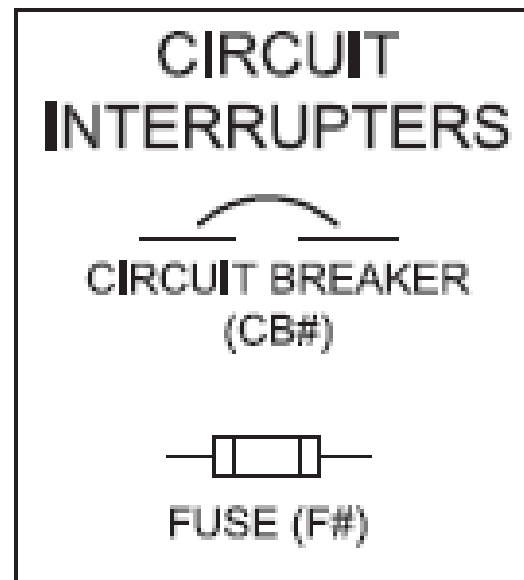
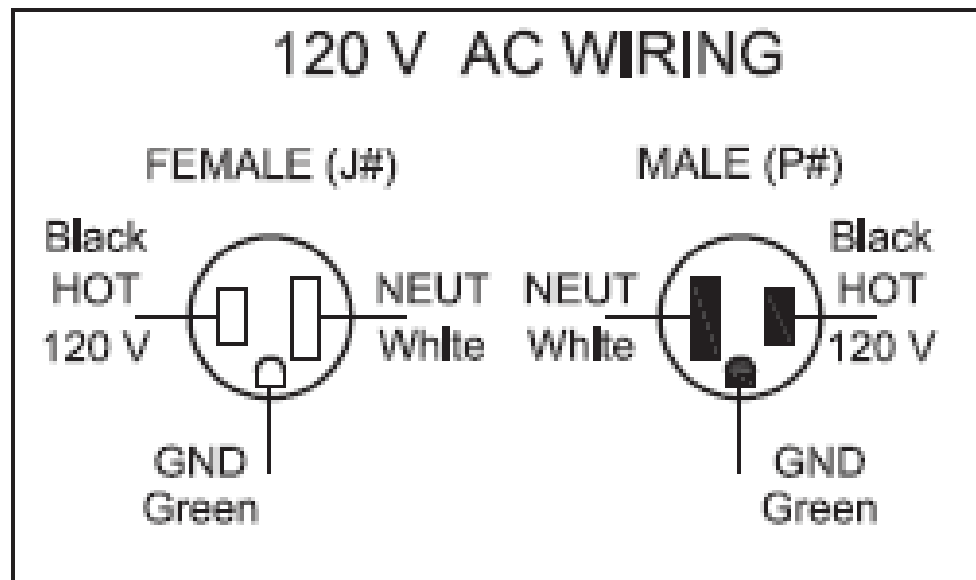
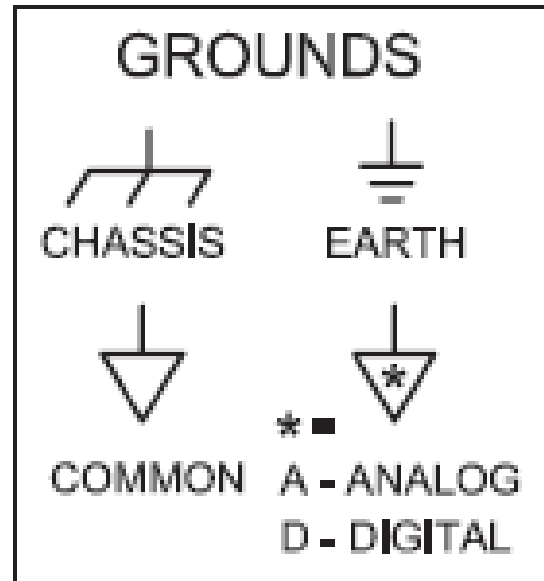


Fig 3.15 – Schematic Symbols (cont., see text)

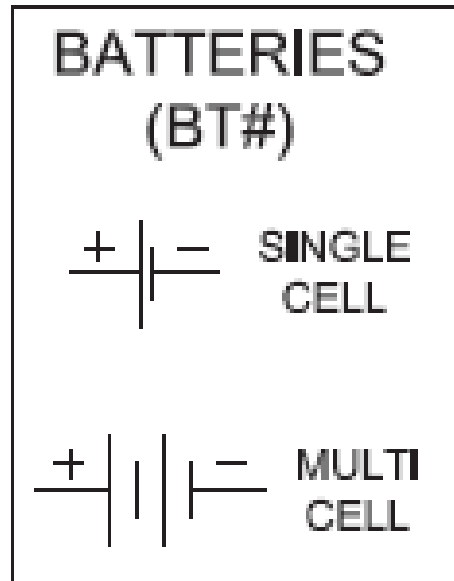

Schematic Diagrams and Symbols

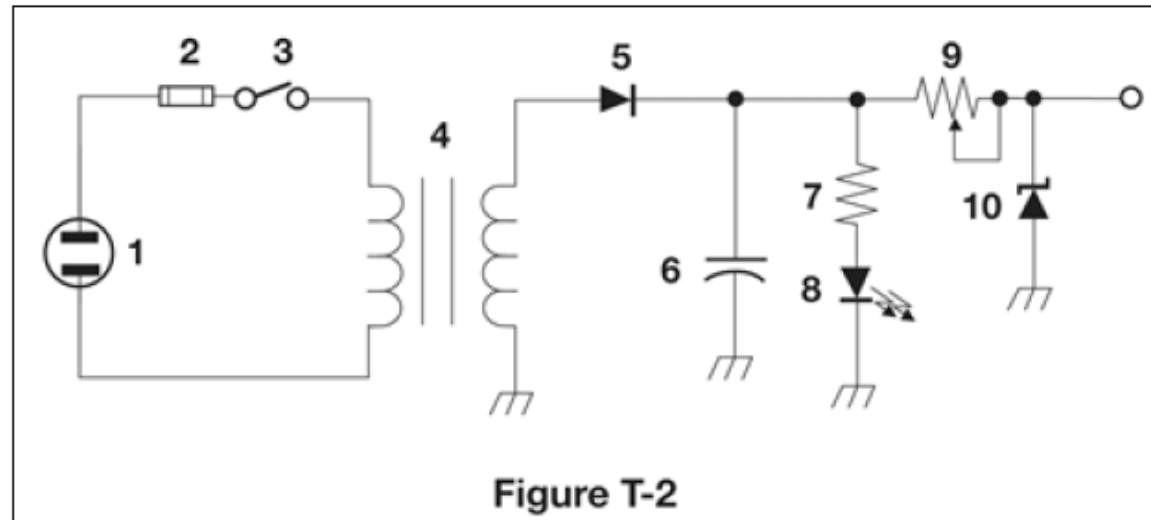- *Symbols* are used when drawing a circuit because there are so many types of components
- *Schematic diagrams* are a visual description of a circuit and its components that uses standardized drawings called *circuit symbols*
 - Shows how the components are connected electrically



Next Week

- Please read chapters in the ARRL Book
 - **Ch 4:** Propagation, Antennas and Feed Lines (**Ch 4** in <https://hambook.org>)
 - **Ch 5:** Amateur Radio Equipment (**Ch 6** in <https://hambook.org>)
- Also start reviewing question pool, either on paper or <https://hamstudy.org>
 - Subelements from today:
 - **T5** – Electrical Principles
 - **T6** – Electronic and Electrical Components
 - Question pool is in the back of the book, and on ARRL website
 - <https://arrl.org/question-pools> (look for the Technician Class Question Pool)
- Slides: <https://tinyurl.com/mcarc-intro-to-ham>
- Radio office hours: Thursdays 7pm-8pm, PMC Condor Room
- Email: kk6dzw@arrl.net